

Problem 6-22

Find the leakage impedance of the 480V, 40 kVA, 3-phase transformer --

$$X_{L1} = 0.03 \times \frac{\left(\frac{480}{\sqrt{3}}\right)^2}{\left(\frac{40 \times 10^3}{3}\right)} = 0.1728 \Omega$$

$$\therefore L_1 = \frac{0.1728}{\omega} \simeq 458 \mu\text{H}$$

From problem 6-21

$$L_{s2} = 20 \mu\text{H} + 458 \mu\text{H} = 478 \mu\text{H}$$

$$\text{and } L_s = L_{s1} + L_{s2} = 73.34 + 478 = 551.34 \mu\text{H}$$

From Eq. 6-55

$$525 = 1.35 \times 460 \times \cos\alpha - \frac{3 \times 377 \times 551.34 \times 10^{-6}}{\pi} \times 47.6$$

$$\therefore \alpha = 30.6^\circ$$

$$u = \frac{2\omega L_s I_d}{\sqrt{2} V_{LL} \sin\alpha} = 59.75 \times 10^{-3} \text{ rad}$$

From Eq. 6-67

$$t_{\text{notch}} = \frac{u}{\omega} = 158.5 \mu\text{s}$$

$$\rho = \frac{L_{s1}}{L_{s1} + L_{s2}} = \frac{73.34}{551.34} = 13.3\%$$

$$\text{deep notch area } A_n = 2\omega(L_s)I_d$$

From Eq. 6-65

$$= 19.79 \text{ V-rad} = 52,487 \text{ V-}\mu\text{s}$$

At the point of common coupling

$$A_{n_{cc}} = \rho A_n = 0.133 \times 52,487 \simeq 6980 \text{ V-}\mu\text{s} \text{ (same as in problem)}$$

Comparing the results with the limits in Table 6-2, the factor ρ now (as compared to the system in Problem 6-21) is acceptable for dedicated and general systems. As before, the line-notch area is acceptable for all systems.