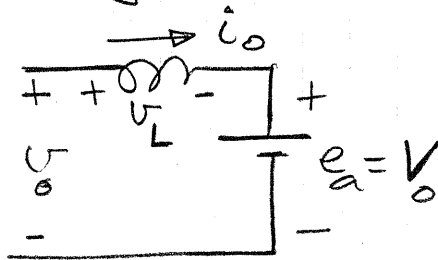


Problem 7-22

In the circuit of Fig. 7-27, $R_a \approx 0$.

Consider the waveforms in Fig. 7-28 under steady state conditions.



during D_1 : T_A^+ , T_B^- ON

during D_2 : T_A^- , T_B^+ ON

$$\Delta I_L = \frac{V_d - V_o}{L_a} D_1 T_s$$

From Eq. 7-74

$$D_1 = \frac{1}{2} \left(1 + \frac{V_o}{V_d} \right)$$

$$\therefore \Delta I_L = \frac{T_s V_d}{2 L_a} \left(1 + \frac{V_o}{V_d} \right) \left(1 - \frac{V_o}{V_d} \right)$$

$$\frac{d(\Delta I_L)}{d\left(\frac{V_o}{V_d}\right)} = \frac{T_s V_d}{2 L_a} \left(-2 \frac{V_o}{V_d} \right) \underset{\text{(set to)}}{=} 0 \quad \therefore \text{maximum occurs at } \frac{V_o}{V_d} = 0.$$

Using $\frac{V_o}{V_d} = 0$ in the equation for ΔI_L ,

$$(\Delta I_L)_{\text{maximum}} = \frac{T_s V_d}{2 L_a} = \frac{V_d}{2 L_a f_s}$$

