

Problem 8-5

peak ripple current = 2.45A (Problem 8-2, Square-Wave)

= 0.98A (Problem 8-3, PWM)

= 2.33A (Problem 8-4, Voltage Cancellation)

The peak ripple current in the PWM is the lowest.