

Problem 5-13


The simulation in part a results in $V_d = 153.04V$.
Therefore, for a power of 1 kW, the following values are calculated:

$$R_{\text{Load}} = \frac{V_d^2}{1000W} = 23.42\Omega \text{ in part b}$$

and

$$I_{\text{Load}} = \frac{1000W}{V_d} = 6.534A$$

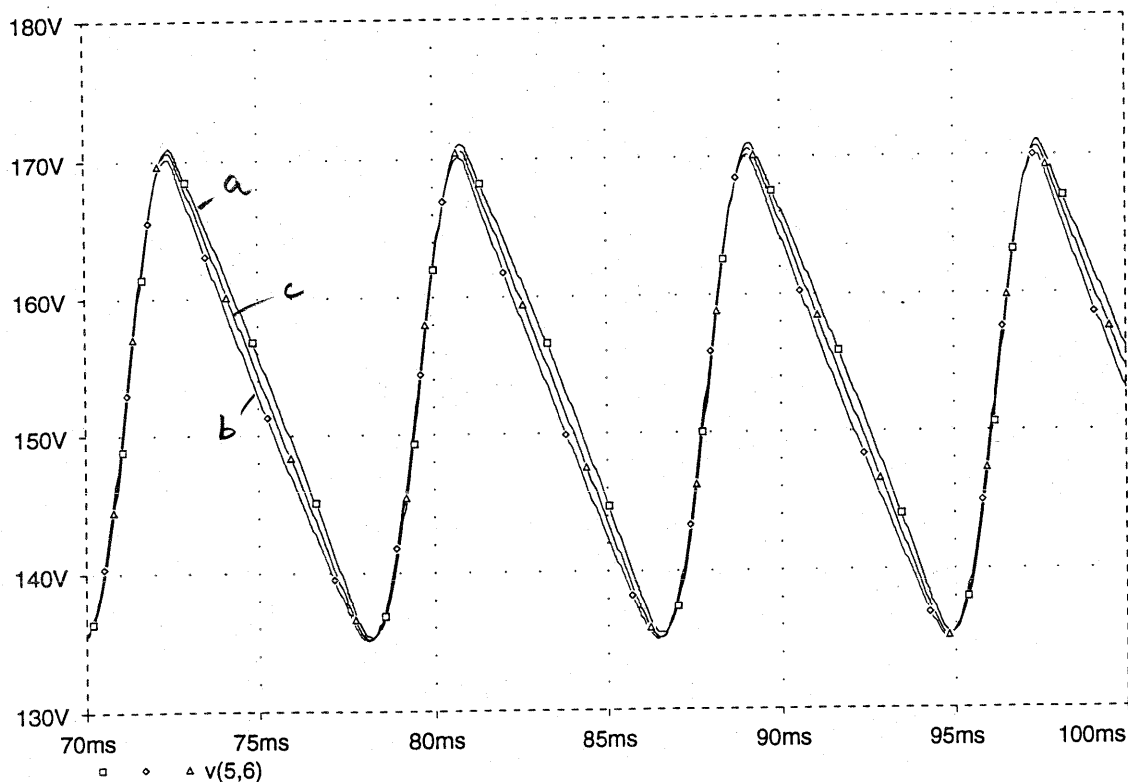To compare results from these three parts, all cases are run in the same file, as the listing indicates. The waveforms are very similar.



```

Prob5_13a
* Single-Phase, Diode-Bridge Rectifier
.LIB PWR_ELEC.LIB
.PARAM FREQ = 60.0Hz
*
LS      1  2  1mH
RS      2  3  0.4
*
rdc     4  5  1u
GDC     5  6  VALUE={1000/V(5,6)}
CD      5  6  1000uF IC=160V
*
XD1     3  4  DIODE_WITH_SNUB
XD3     0  4  DIODE_WITH_SNUB
XD2     6  0  DIODE_WITH_SNUB
XD4     6  3  DIODE_WITH_SNUB
*
VS      1  0  SIN(0 170V {FREQ} 0 0 0)
*
.TRAN   50us  100ms  0s  50us  UIC
.PROBE
.FOUR   60.0  v(1) i(LS)  i(rdc)  v(5,6)
.END
Prob5_13b
* Single-Phase, Diode-Bridge Rectifier
.LIB PWR_ELEC.LIB
.PARAM FREQ = 60.0Hz
*
LS      1  2  1mH
RS      2  3  0.4
*
rdc     4  5  1u
RLOAD   5  6  23.42
CD      5  6  1000uF IC=160V
*
XD1     3  4  DIODE_WITH_SNUB
XD3     0  4  DIODE_WITH_SNUB
XD2     6  0  DIODE_WITH_SNUB
XD4     6  3  DIODE_WITH_SNUB
*
VS      1  0  SIN(0 170V {FREQ} 0 0 0)
*
.TRAN   50us  100ms  0s  50us  UIC
.PROBE
.FOUR   60.0  v(1) i(LS)  i(rdc)  v(5,6)
.END
Prob5_13c
* Single-Phase, Diode-Bridge Rectifier
.LIB PWR_ELEC.LIB
.PARAM FREQ = 60.0Hz
*
LS      1  2  1mH
RS      2  3  0.4
*
rdc     4  5  1u
ILOAD   5  6  6.534A
CD      5  6  1000uF IC=160V
*
XD1     3  4  DIODE_WITH_SNUB
XD3     0  4  DIODE_WITH_SNUB
XD2     6  0  DIODE_WITH_SNUB
XD4     6  3  DIODE_WITH_SNUB
*
VS      1  0  SIN(0 170V {FREQ} 0 0 0)
*
.TRAN   50us  100ms  0s  50us  UIC
.PROBE
.FOUR   60.0  v(1) i(LS)  i(rdc)  v(5,6)
.END

```

Note: No blank lines between 3 parts.