

Problem 5-28

In the single-phase rectifier:

$$V_{d, \max} = 138.6 \text{ V}$$

$$V_{d, \min} = 107.3 \text{ V}$$

$$\Delta V_d \text{ p-p} = 31.3 \text{ V}$$

$$V_d(\text{avg}) = 122.2 \text{ V}$$

$$\% \Delta V_d \text{ p-p} = \frac{31.3}{122.2} \times 100$$

$$\phi_i = -24.31^\circ, \quad \text{THD}_i = 45.34\%$$

$$= 25.6\%$$

$$\therefore \text{DPF} = 0.911 \text{ (lagging)} \quad \text{PF} = 0.83 \text{ [using Eq 3-45]}$$

$$\text{Energy Storage (based on } V_d(\text{avg}) \text{)} = \frac{1}{2} C V_{d, \text{avg}}^2 = 8.21 \text{ W-s}$$

$C = 24$

Three-Phase Rectifier

By trial-and-error, it is determined that $C_d = 275 \mu F$ results in approximately the same energy stored as in the 1-phase case. However, the simulation becomes unstable with a constant power load. Therefore, it is represented by $R_{Load} = 14.8 \Omega$.

$$V_{d, \max} = 285.9 V$$

$$V_{d, \min} = 257.8 V$$

$$V_{d, \text{avg}} = 271.4 V$$

$$\Delta V_{d \text{ p-p}} = 28.1 V$$

$$\% \Delta V_{d \text{ p-p}} = 10.35 \%$$

$$\phi_1 = -15.64^\circ (\text{lag}), \quad THD_c = 43.5 \%$$

$$DPF = 0.963 \text{ (lagging)}$$

$$PF = 0.883$$

Comparing the two results, the 3-phase rectifier results in substantially less dc-voltage ripple and also operates at a better power factor.