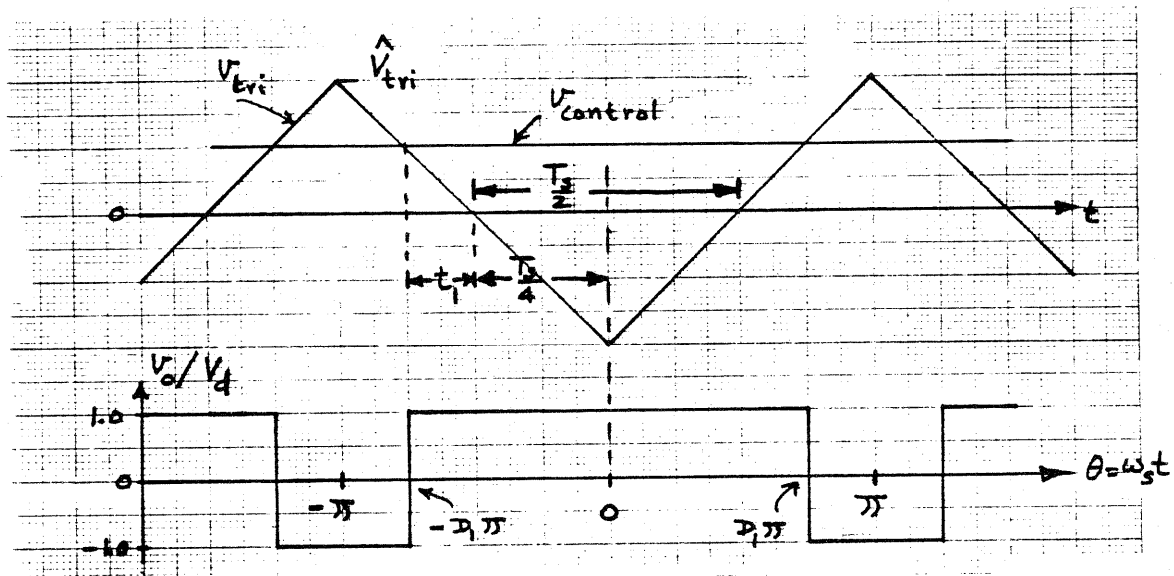


# FULL-BRIDGE CONVERTER

## Problem 7-18



Even function:  $f(t) = -f(t)$

||

From Eqs. 7-71 and 7-72

$$t_1 + \frac{T_s}{4} = \frac{D_1 T_s}{2} \therefore \omega_s \left( t_1 + \frac{T_s}{4} \right) = \pi D_1$$

For an even function:

$$f(t) = \frac{1}{2} a_0 + \sum_{n=1}^{\infty} a_n \cos n\omega_s t$$

$$a_n = \frac{4}{T_s} \int_0^{T_s/2} f(t) \cdot \cos(n\omega_s t) \cdot dt$$

$$= \frac{4}{\omega_s T_s} \int_0^{\omega_s T_s/2} f(\omega_{st}) \cdot \cos(n\omega_{st}) \cdot d(\omega_{st}) = \frac{2}{\pi} \int_0^{\pi} f(\theta) \cdot \cos(n\theta) \cdot d\theta$$

where  $\omega_s T_s = 2\pi$  and  $\omega_{st} = \theta$ .  $D_1$  is the duty-ratio as defined in Eq. 7-72.

$$\therefore a_0 = \frac{2}{\pi} \left[ \int_0^{D_1\pi} 1 \cdot d\theta + \int_{D_1\pi}^{\pi} (-1) \cdot d\theta \right] = \frac{2}{\pi} [D_1\pi - \pi + D_1\pi] = 2[2D_1 - 1]$$

From Eq. 7-72,  $D_1 = 0.75$

$$\therefore \frac{V_o}{V_d} = \frac{1}{2} a_0 = 0.5$$

$$\begin{aligned} a_n &= \frac{2}{\pi} \left[ \int_0^{D_1\pi} 1 \cdot \cos(n\theta) \cdot d\theta + \int_{D_1\pi}^{\pi} (-1) \cdot \cos(n\theta) \cdot d\theta \right] \\ &= \frac{2}{n\pi} [\sin(D_1 \cdot n\pi) - \sin(n\pi) + \sin(D_1 n\pi)] = \frac{2}{n\pi} [2 \cdot \sin(D_1 n\pi)] \\ &= \frac{4}{n\pi} \sin(D_1 n\pi) \end{aligned}$$

$$\therefore \frac{\hat{V}_{o,n}}{V_d} = \frac{4}{n\pi} \sin D_1 n\pi \quad n = 1, 2, 3, \dots$$

( $n$  represents the  $n$ th multiple of the switching frequency  $f_s$  and  $\hat{V}_{o,n}$  is the peak amplitude)

$n$	$\frac{\hat{V}_{o,n}}{V_d}$ ( $D_1 = 0.75$ )
1	0.9
2	0.64
3	0.3
4	0
5	0.18
6	0.212

Note: We are asked to assume that  $i_o(t) \approx I_o$ . Therefore,  $[i_d(t)/I_o]$  waveform will be identical to the  $[v_o(t)/V_d]$  waveform shown earlier.

Also, the Fourier components of  $[i_d(t)/I_o]$  will be identical to those shown in the Table on the left.