

Problem 6-21

transformer: 3ϕ , 500 KVA, 480 V_{LL}, leakage reactance $X_{Ls1} \approx \text{impedance} = 6\%$

Find L_{s1} ____

$$X_{Ls1} = 0.06 \frac{\left(\frac{480V}{\sqrt{3}}\right)^2}{\left(\frac{500 \text{ KVA}}{3}\right)} = 27.65 \text{ m}\Omega$$

$$L_{s1} = X_{Ls1} / \omega = \frac{27.65 \text{ m}\Omega}{377} = 73.34 \text{ }\mu\text{h}$$

Find L_{s2} ____

$$L_{s2} = 200\text{ft} \times 0.1 \frac{\mu\text{h}}{\text{ft}} = 20 \text{ }\mu\text{h}$$

find α ____

$$L_s = L_{s1} + L_{s2} = 93.34 \text{ }\mu\text{H}$$

$$V_d = 525\text{V}$$

$$V_{LL} = 460 \text{ V}$$

$$I_d = \frac{25\text{kW}}{525\text{V}} = 47.6\text{A}$$

$$V_d = 1.35 V_{LL} \cos\alpha - \frac{3\omega L_s}{\pi} I_d$$

$$\therefore \alpha = 32^\circ$$

Using Eq. 6-67

$$u = \frac{2\omega L_s I_d}{\sqrt{2} V_{LL} \sin\alpha} = 971.8 \times 10^{-5} \text{ rad}$$

$$\therefore t_{\text{notch}} = \frac{u}{\omega} \approx 25.78 \text{ }\mu\text{s}$$

Using Eq. 6-68

$$\rho = \frac{L_{s1}}{L_{s1} + L_{s2}} = \frac{73.3}{73.3 + 20} = 0.786 = 78.6\%$$

Using Eq. 6-65

$$\text{deep notch area } A_n = 2\omega(L_{s1} + L_{s2})I_d = 3.35 \text{ V-rad} = 8886 \text{ V-}\mu\text{s}$$

At the point of common coupling, the deep-notch area is

$$A_{ncc} = \rho A_n \simeq 6980 \text{ V-}\mu\text{s}$$

Comparing the results with the limits given in Table 6-2, $\rho = 78.6\%$ exceeds the limits for all class of applications. However, the line-notch area of $6980 \text{ V-}\mu\text{s}$ is within the limits for all class of applications.