

Problem 3-2

$$(9) \quad v = \sqrt{2} 120 \cos \omega t, \quad i = \sqrt{2} \cos(\omega t - 30^\circ)$$

$$p(t) = v(t) \cdot i(t)$$

$$\phi = 30^\circ$$

$$i_p = (\sqrt{2} I \cos \phi) \cos \omega t$$

$$Eq \quad 3-12$$



$$i_q = (\sqrt{2} I \sin \phi) \sin \omega t$$

$$Eq \quad 3-13$$

$$p_1 = v \cdot i_p$$

$$p_2 = v \cdot i_q$$

3-1

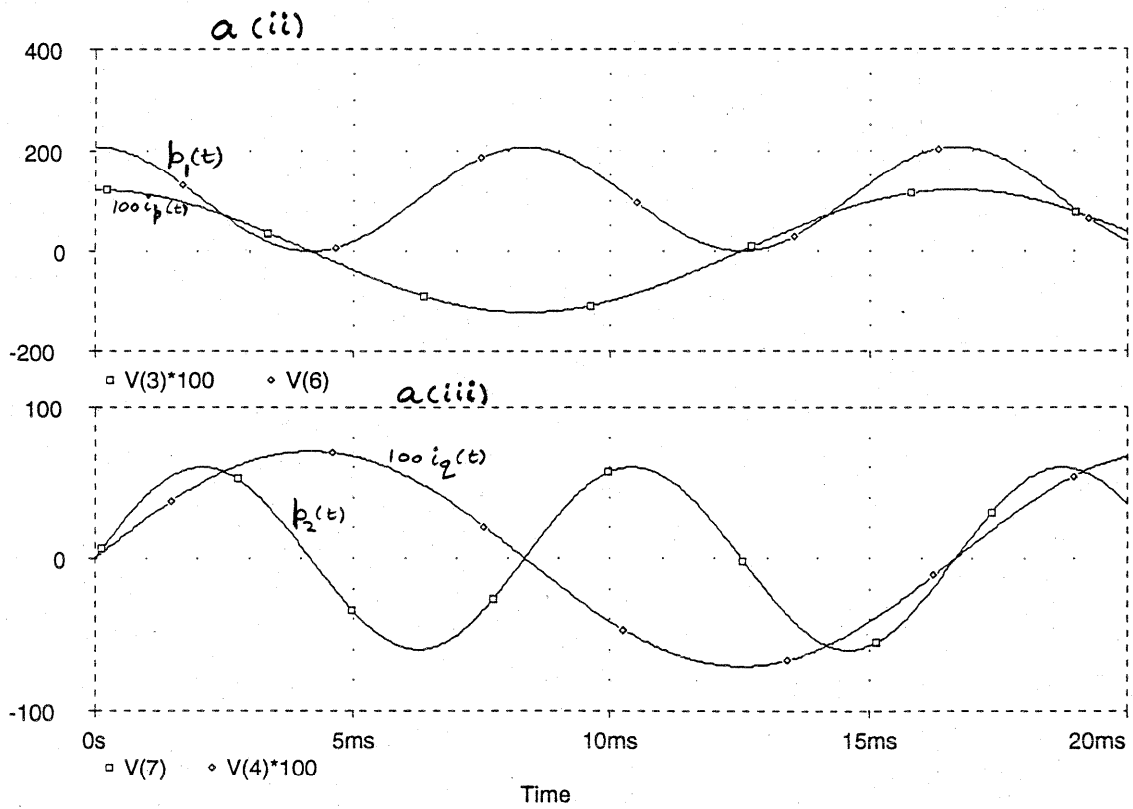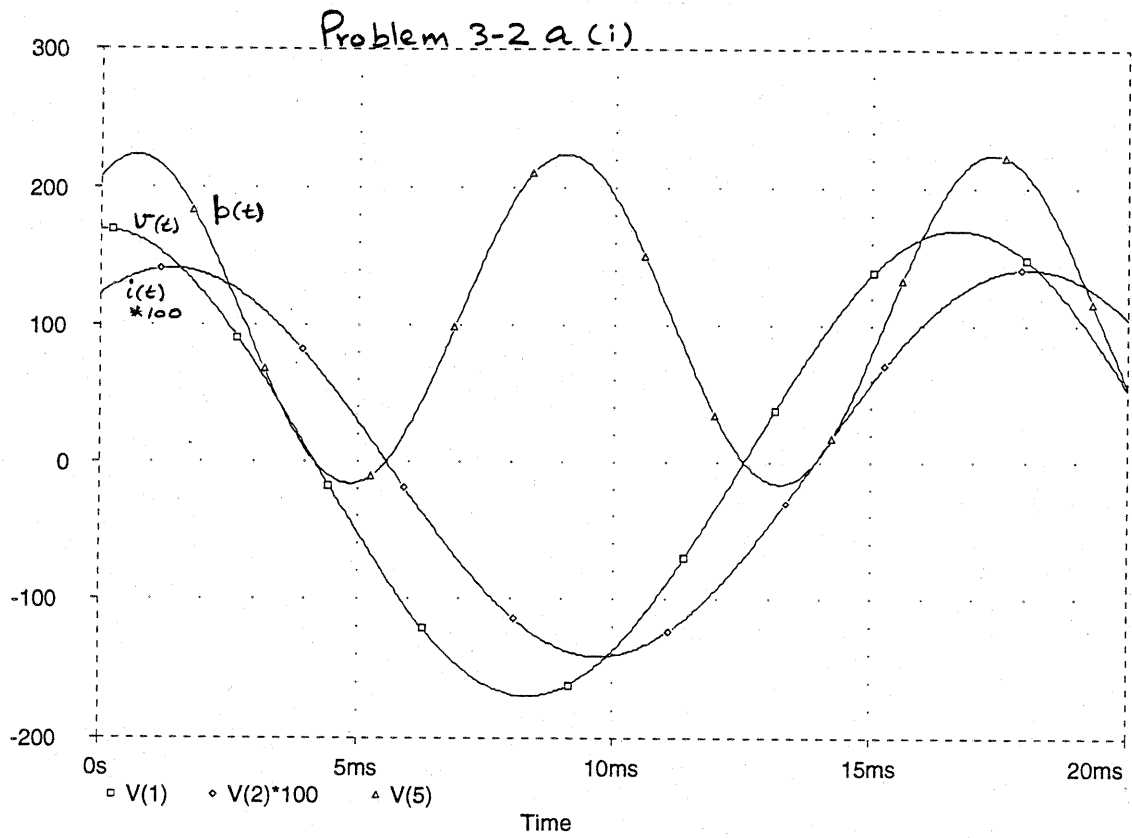

$$(b) \quad P = VI \cos \phi = 120 \times 1 \times \cos 30^\circ = 103.92 \text{ W}$$

$$(c) \quad Q = VI \sin \phi \quad \text{Eq 3-14}$$

$$= 120 \times 1 \times \sin 30^\circ$$

$$= 60 \text{ VA}$$

Also from peak of $p_2(t)$ in part a(iii).

$$(d) \quad \text{PF} = \cos \phi = 0.866 \text{ (lagging)}$$

The load is inductive and it draws positive vars from the source.