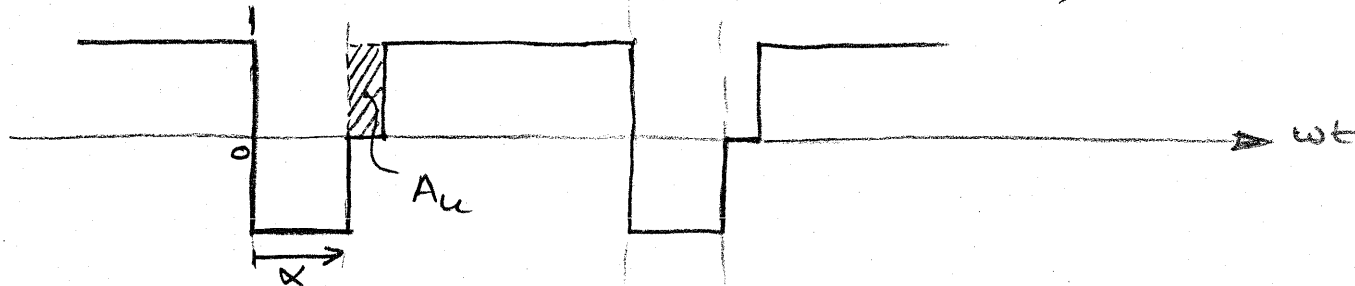


# Problem 6-4

$$\text{at } \alpha = 135^\circ, \frac{V}{d\alpha} = -1001$$

(a) In the above circuit in the presence of  $L_s$ ,



$$A_u = \omega L_s [I_d - (-I_d)] = 2\omega L_s I_d$$

$$\therefore V_d = \frac{V}{d\alpha} - \frac{A_u}{\pi}$$

(in Problem 6-3)

6-4


$u$  is independent of  $\alpha$  here because the commutation voltage is the same, independent of  $\alpha$ .

∴

$$V_d = V_{\text{ampl}} \left( 1 - \frac{2\alpha}{\pi} \right) - \frac{2\omega L_s}{\pi} I_d$$

in radians

To calculate  $u$ :

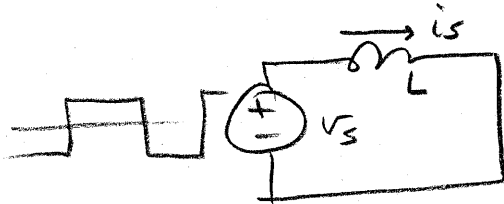

Circuit during the commutation interval.  $V_s = V_{\text{ampl}}$

$$L_s \frac{di_s}{dt} = V_s$$

$$\therefore V_{\text{ampl}} \int_{\alpha}^{\alpha+u} d(\omega t) = \omega L_s \int_{-I_d}^{I_d} di_s$$

$$\therefore V_{\text{ampl}} [(\alpha+u) - \alpha] = 2\omega L_s I_d$$

$$\text{or } u = \frac{2\omega L_s I_d}{V_{\text{ampl}}}$$

(b)

Substituting values

$$\alpha = 45^\circ,$$

$$V_d = 92.8 \text{ V},$$

$$u = 6.48^\circ$$

$$\alpha = 135^\circ,$$

$$V_d = -107.2 \text{ V},$$

$$u = 6.48^\circ$$