
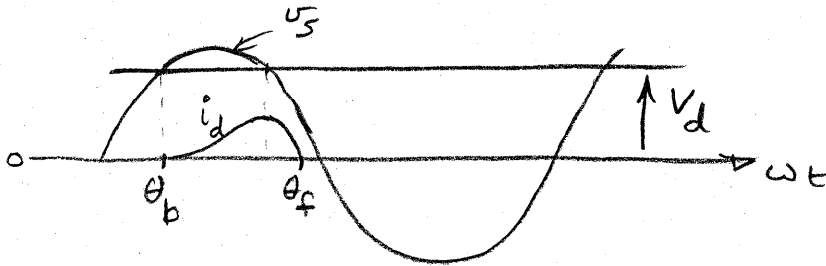


Problem 5-17

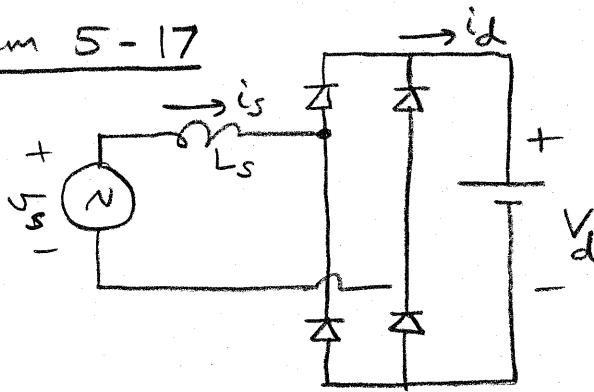

$$\theta_b < \theta < \theta_f$$

$$\begin{aligned} i_d(\theta) &= \frac{1}{\omega L_s} \int_{\theta_b}^{\theta} [\sqrt{2} V_s \sin \omega t \cdot d(\omega t) - V_d] \cdot d(\omega t) \\ &= \sqrt{2} \left(\frac{V_s}{\omega L_s} \right) \int_{\theta_b}^{\theta} \sin \omega t \cdot d(\omega t) - \frac{V_d}{V_s} \cdot \left(\frac{V_s}{\omega L_s} \right) (\theta - \theta_b) \end{aligned}$$

$$\therefore \frac{i_d(\theta)}{I_{\text{short circuit}}} = \sqrt{2} (\cos \theta_b - \cos \theta) - \frac{V_d}{V_s} (\theta - \theta_b)$$

$$\text{where, } I_{\text{short circuit}} = \frac{V_s}{\omega L_s}$$

For a specific value of $\left(\frac{V_d}{V_s} \right)$, the following can be uniquely calculated:

θ_b , θ_f , and from the above equation

$$\frac{i_d(\theta)}{I_{\text{short circuit}}} \text{ for } \theta_b < \theta < \theta_f. \quad \text{Since } I_d = \left[\int_{\theta_b}^{\theta_f} i_d(\theta) \cdot d\theta \right] / \pi,$$

$$\frac{I_d}{I_{\text{short circuit}}} \text{ can also be uniquely calculated.}$$

Since $i_d(\theta)$ is specified, PF, DPF, THD and CF can be uniquely obtained.