
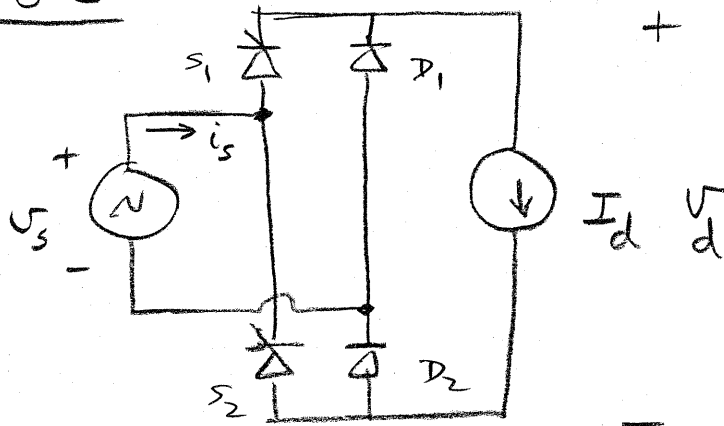


Problem 6-5

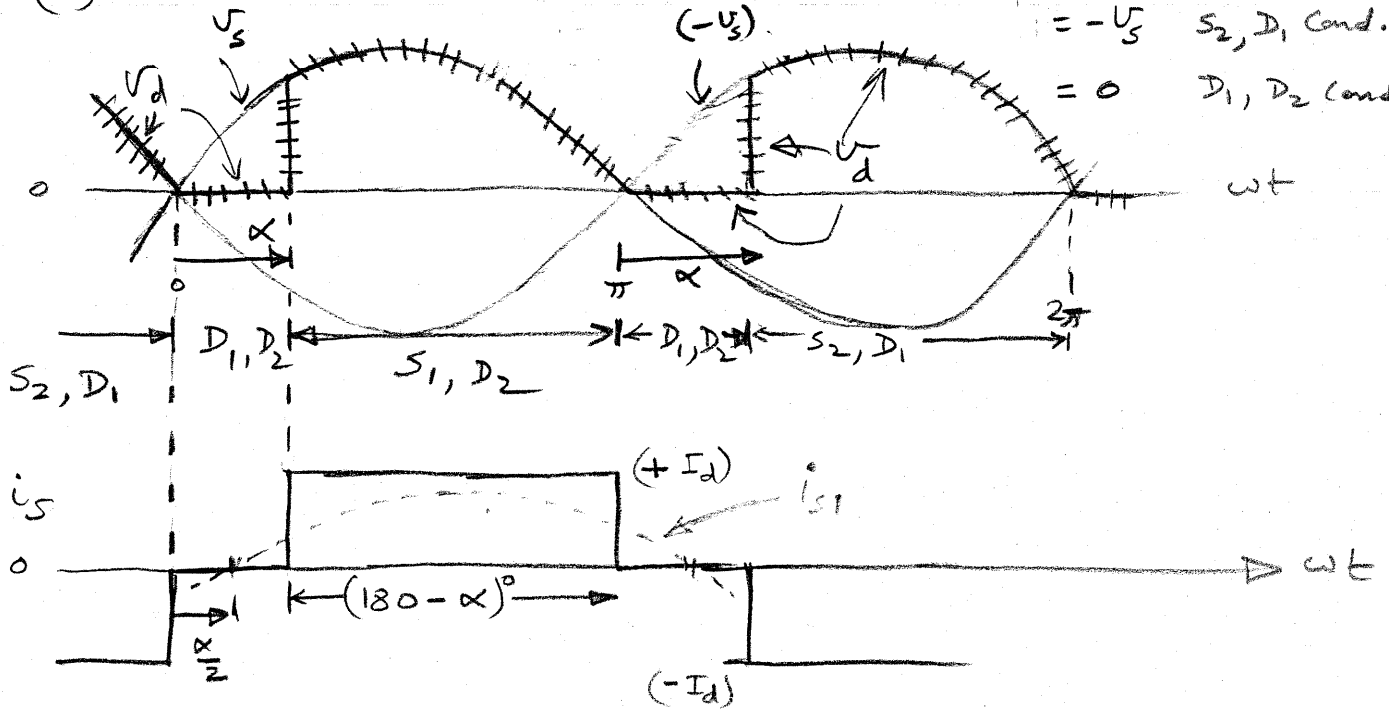

(a)



$$V_{d0} = 0.9 V_s$$

$$V_{d\alpha} = \frac{\sqrt{2} V_s}{\pi} \int_{\alpha}^{\pi} \sin \omega t \cdot d(\omega t) = \frac{\sqrt{2} V_s}{\pi} [\cos \alpha + 1]$$

$$DPF = \cos \left(\frac{\alpha}{2} \right) \text{ by observation of } i_s \text{ waveform}$$

$$I_s = I_d \sqrt{\frac{180^\circ - \alpha}{180^\circ}} ; I_{s1} \text{ can be calculated by equating power:}$$

$$V_s I_{s1} \cdot DPF = V_{d\alpha} I_d$$

$$I_{s1} = \frac{V_{d\alpha} I_d}{V_s \cos \frac{\alpha}{2}} \quad DPF$$

$$(b) \quad V_{d\alpha} = \frac{1}{2} V_{d0}$$

$$\therefore \frac{\sqrt{2} V_s}{\pi} (1 + \cos \alpha) = \frac{1}{2} \times 0.9 V_s$$

$$\alpha \quad \cos \alpha = \frac{\pi \times 0.9}{2\sqrt{2}} - 1$$

$$\therefore \alpha = 90^\circ$$

$$\therefore \text{DPF} = \cos\left(\frac{\alpha}{2}\right) = 0.707$$

$$I_s = I_d \sqrt{\frac{180 - 90}{180}} = 0.707 I_d$$

$$I_{s1} = \frac{0.5 \times 0.9 V_s}{V_s \cos\left(\frac{90^\circ}{2}\right)} I_d = 0.636 I_d$$

$$\therefore \text{PF} = \frac{I_{s1}}{I_s}, \quad \text{DPF} = 0.636$$

$$\begin{aligned} \% \text{THD}_i &= \frac{\sqrt{I_s^2 - I_{s1}^2}}{I_{s1}} \% = \frac{\sqrt{0.707^2 - 0.636^2}}{0.636} \times 100 \\ &= 48.55 \% \end{aligned}$$

(c) In a full-bridge converter,

$$V_{d\alpha} = V_{d0} \cos \alpha \quad [\text{Eq. 6-6}]$$

$$\therefore \text{for } V_{d\alpha} = 0.9 V_0, \quad \alpha = 60^\circ$$

$$\text{DPF} = \cos \alpha = 0.5 \quad [\text{Eq. 6-16}]$$

$$\text{PF} = 0.9 \cos \alpha = 0.45 \quad [\text{Eq. 6-17}]$$

$$\% \text{THD}_L = 48.43 \%$$

(d) Comparison of (b) and (c) shows that the Power Factor is better in the half-controlled converter.