

## Cuk CONVERTER

### Problem 7-17


When the switch is off:  $i_{c1} = i_{L1}$

When the switch is on:  $i_{c1} = -i_{L2}$

Assume a constant  $i_{L1} = I_d = 0.5A$ , and a constant  $i_{L2} = I_o = 1A$ .

$D = 0.333$  (Example 7-3)

7-10

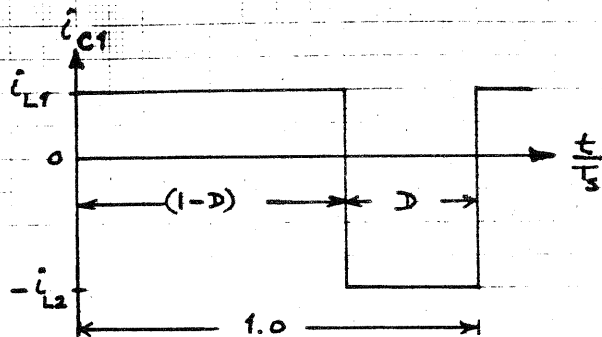

$$\therefore I_{C1}(\text{rms}) \approx \sqrt{\frac{(0.5^2 \times 0.667) + 1^2 \times 0.333}{1}} = 0.707\text{A}$$