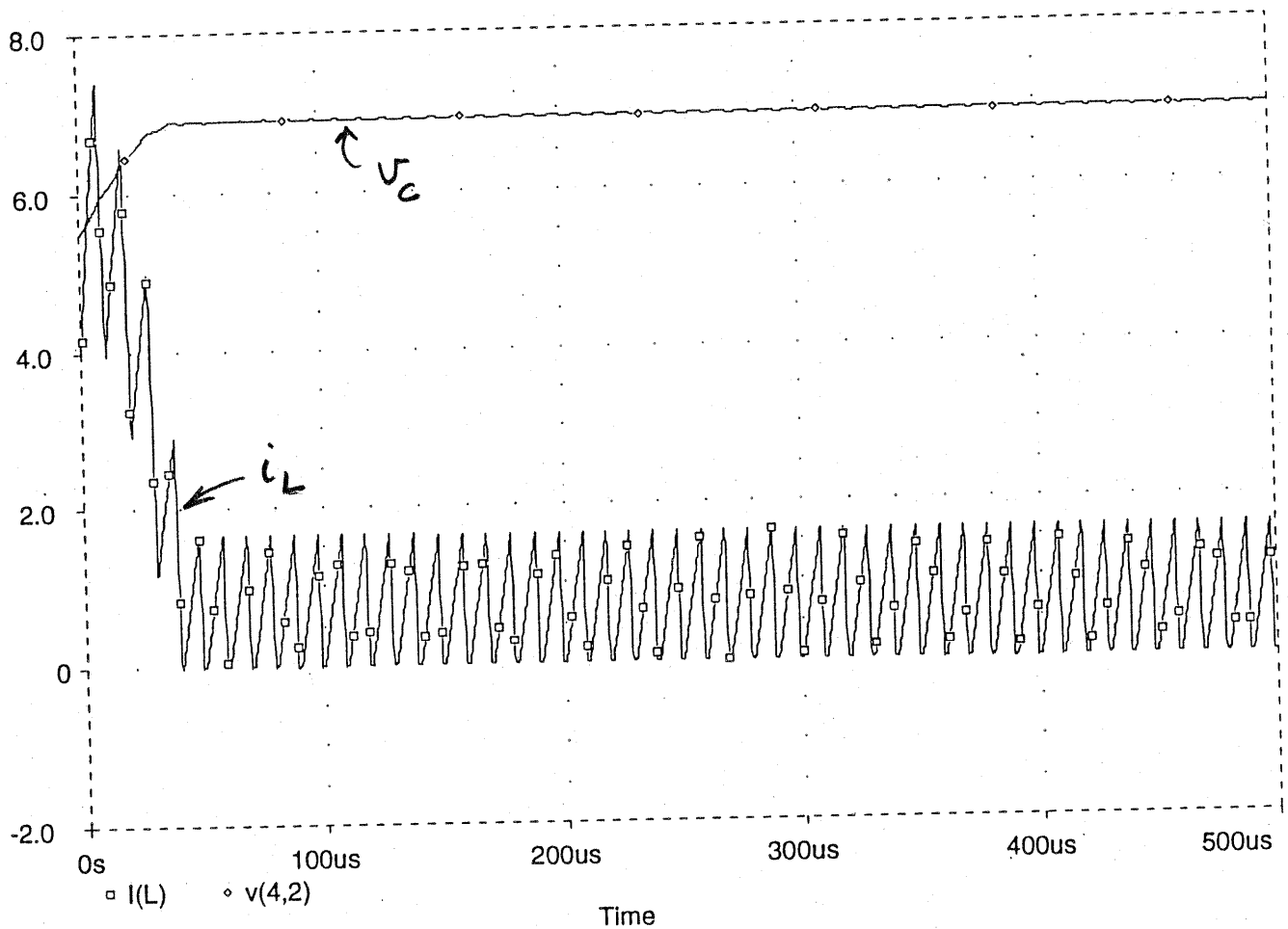


Problem 4-8

PSpice Example

Date/Time run: 10/11/94 18:26:56

Temperature: 27.0



The inductor current i_L becomes discontinuous at light load ($R_{LOAD} = 10.0 \Omega$).