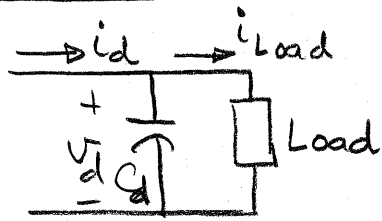


Problem 5-16



Representing the load by a constant instantaneous power $p_d(t) = 1000 \text{ W}$ has the following consequences:

As V_d increases, i_{Load} goes down instantaneously. This corresponds to a negative incremental resistance (in a normal resistance as the voltage across it goes up, the current also increases). Therefore, such a load representation introduces a negative damping. Loads such as switch-mode, regulated dc power supplies discussed in chapter 10 are examples of such loads.

With the load represented as above, the system with $C_d = 200 \mu\text{F}$ in part (a) is operated and the dc voltage collapses to zero and the PSpice simulation ends with a convergence error. In part (b) with $C_d = 500 \mu\text{F}$, the simulation becomes unstable with unsymmetric current waveforms during the negative half-cycles,

Compared to the positive half-cycles. This becomes very clear if the simulation is run upto 200ms.

The results with C_d of 1000 μF and 1500 μF are tabulated below based on the following observations from the PSpice output:

$$\underline{C_d = 1000 \mu\text{F}}$$

$$V_{d,\min} = 131.1 \text{ V}$$

$$V_{d,\max} = 164.5 \text{ V}$$

$$\phi_i = -15.3^\circ (i_s \text{ lags } v_s)$$

$$\text{THD}_i = 72.3\%$$

(based on harmonics upto the 25th)

$$\left[\text{From Eq. 3-45, } \text{PF} = \frac{1}{\sqrt{1 + \text{THD}_i^2}} \cdot \text{DPF} \right]$$

$$\text{DPF} = 0.965 (\text{lag})$$

$$\therefore \text{PF} = 0.782$$

$$\Delta V_{d\text{p-p}} = 33.4 \text{ V}$$

$$\underline{C_d = 1500 \mu\text{F}}$$

$$V_{d,\min} = 133.8 \text{ V}$$

$$V_{d,\max} = 156.0 \text{ V}$$

$$\phi_i = -17.81^\circ$$

$$\text{THD}_i = 69.7\%$$

$$\text{DPF} = 0.952 (\text{lag})$$

$$\text{PF} = 0.781$$

$$\Delta V_{d\text{p-p}} = 22.2 \text{ V}$$

As a continuation of this problem, the load

is represented in the attached PSpice listing by a $20\ \Omega$ resistor and the resulting dc-voltage V_d waveforms are plotted for the given 4 values of C_d .

```

Prob5_16A modified to represent load with a resistance
* Single-Phase, Diode-Bridge Rectifier
.LIB PWR_ELEC.LIB
.PARAM FREQ = 60.0Hz
.PARAM CVALUE = 1
*
LS      1  2  2mH
RS      2  3  0.4
*
rdc     4  5  1u
RLOAD   5  6  20
CD       5  6  {CVALUE} IC={160 + (CVALUE - 1000u)/100u}
*
XD1     3  4  DIODE_WITH_SNUB
XD3     0  4  DIODE_WITH_SNUB
XD2     6  0  DIODE_WITH_SNUB
XD4     6  3  DIODE_WITH_SNUB
*
VS      1  0  SIN(0 170V {FREQ} 0 0 0)
*
.TRAN   50us  200ms  0s  50us  UIC
.PROBE
.FOUR   60.0  25  v(1) i(LS) i(rdc) v(5,6)
.STEP PARAM CVALUE LIST 200u,500u,1000u,1500u
.END

```

