

Problem 7-11

$$V_d = 12V, V_o = 24V, L = 150\mu H, C = 470\mu F, f_s = 20kHz$$

From the solution of Problem 7-8

$$I_{oB} = 0.5A$$

$$\therefore I_o = \frac{I_{oB}}{2} = 0.25A$$

From Eq. 7-31

$$I_{oB, \max} = 0.074 \frac{T_s V_o}{L} = 0.592A$$

From Eq. 7-38

$$D = \left[\frac{4}{27} \left(\frac{V_o}{V_d} \right) \left(\frac{V_o}{V_d} - 1 \right) \frac{I_o}{I_{oB, \max}} \right]^{1/2}$$

$$= \left[\frac{4}{27} (2) (1) \frac{0.25}{0.592} \right]^{1/2} = 0.354$$

From the expression derived in Problem 7-10

$$\Delta V_o = \frac{1}{2 \times 150 \times 10^{-6} \times 470 \times 10^{-6}} \frac{(12 \times 0.354 \times 50 \times 10^{-6} - 150 \times 10^{-6} \times 0.25)^2}{(24 - 12)}$$

$$= 18.1mV$$