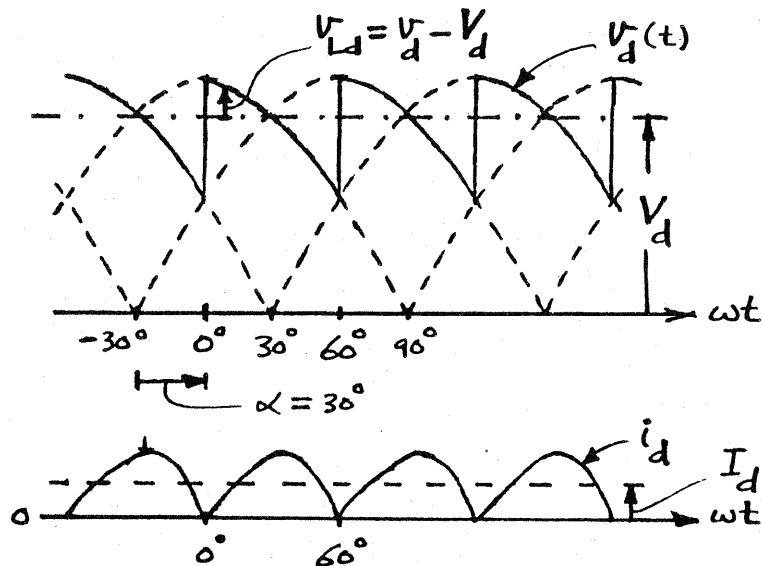


# Problem 6-14



Redefine  $\omega t = 0$  to be at the start of the commutation ( $\alpha = 30^\circ$ ). Then,

$$v_d(\omega t) = \sqrt{2} V_{LL} \cos \omega t \quad 0^\circ < \omega t < 60^\circ$$

$$V_d = 1.35 V_{LL} \cos 30^\circ = 1.169 V_{LL}$$

$$i_d(\omega t) = \frac{1}{\omega L_d} \int v_{Ld} d\omega t$$

$$0^\circ < \omega t < 60^\circ$$

$$= \frac{1}{\omega L_d} (\sqrt{2} V_{LL} \sin \omega t - 1.169 V_{LL} \omega t + K) \quad , \quad K = \text{a constant of integration}$$

Calculate K:

$$i_d(0) = 0 \quad \text{in the figure above}$$

$$\therefore K = 0 \quad \text{and,}$$

$$i_d(\omega t) = \frac{\sqrt{2} V_{LL}}{\omega L_d} (\sin \omega t - 0.8266 \omega t) \quad 0 < \omega t < \frac{\pi}{3}$$

Calculate the average current  $I_d$ :

$$I_d = \frac{1}{\pi/3} \int_0^{\pi/3} i_d d\omega t$$

$$= \frac{3 \sqrt{2} V_{LL}}{\pi \omega L_d} \left[ -\cos \omega t - \frac{0.8266}{2} (\omega t)^2 \right]_0^{\pi/3}$$

$$= \frac{3 \sqrt{2} V_{LL}}{\pi \omega L_d} \left[ -\frac{1}{2} + 1 - 0.4532 \right]$$

Therefore, the minimum dc current  $I_{dB}$  at  $\alpha = 30^\circ$  is

$$I_{dB} = 0.1403 \frac{\sqrt{2}}{\pi} \frac{V_{LL}}{\omega L_d} = 0.0632 \frac{V_{LL}}{\omega L_d} .$$