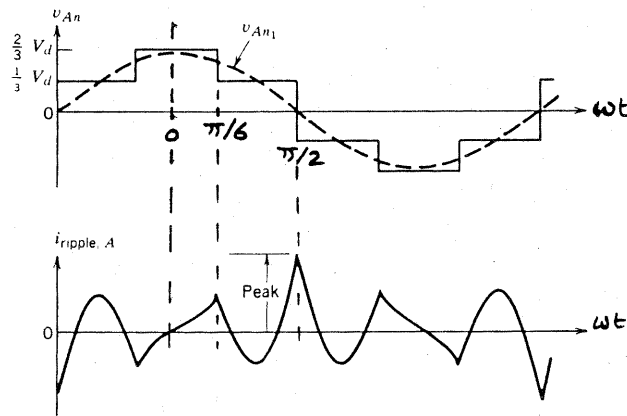


Problem 8-7

Using Eq. 8-58

$$V_d = \frac{\pi}{\sqrt{6}} V_{LL1}(\text{rms}) = \frac{200}{0.78} = 256.51 \text{ V}$$



From Eq. 8-58,

$$\hat{V}_{An1} = \frac{\sqrt{6}}{\pi} \times \frac{\sqrt{2}}{\sqrt{3}} V_d = \frac{2}{\pi} \cdot V_d = 163.3 \text{ V}$$

$$\therefore v_{An1} = 163.3 \cos \omega t$$

$$i_{L,\text{ripple}} = \frac{1}{L} \int_0^t (v_{A_n} - v_{A_{n1}}) \cdot dt = \frac{1}{\omega L} \int_0^{\omega t} (v_{A_n} - v_{A_{n1}}) \cdot d(\omega t)$$

As shown in the figure, the peak ripple current occurs at $\omega t = \pi/2$.

$$\therefore i_{L,\text{ripple}}(\omega t = \frac{\pi}{2}) = \frac{1}{\omega L} \left[\int_0^{\pi/6} \left(2 \cdot \frac{V_d}{3} - \hat{V}_{A_{n1}} \cos \omega t \right) \cdot d\omega t \right]$$

[Note that the ripple current at $\omega t = 0$ is zero in the figure above]

$$+ \int_{\pi/6}^{\pi/2} \left(\frac{V_d}{3} - \hat{V}_{A_{n1}} \cos \omega t \right) \cdot d\omega t]$$

$$= \frac{1}{\omega L} \left[2 \cdot \frac{V_d}{3} \cdot \frac{\pi}{6} + \frac{V_d}{3} \left(\frac{\pi}{2} - \frac{\pi}{6} \right) - \hat{V}_{A_{n1}} \sin \omega t \Big|_0^{\pi/2} \right]$$

$$= \frac{1}{\omega L} \left[\frac{2}{9} \pi V_d - \hat{V}_{A_{n1}} \right] = 0.483 \text{ A (peak ripple current)}$$