

Problem 6-7

$$P_d = 1 \text{ kW}, \quad I_d = 10 \text{ A}, \quad \dot{I}_d \approx I_d$$

$$V_s = 115 \text{ V} (+5\%, -10\%)$$

Calculate L_s :

$$\omega = 2\pi \times 60 = 377 \text{ rad/s}$$

$$\text{Transformer } VA = 1500 \text{ VA}$$

$$\text{rated } V_{pri} = 120 \text{ V}$$

$$\text{rated } I_{pri} = 1500/120 = 12.5 \text{ A}$$

$$Z_{base} = V_{pri}/I_{pri} \text{ (rated)} = 9.6 \Omega$$

$$\omega L_s = (8\%) Z_{base}$$

$$\text{or } L_s = 0.08 \times 9.6 / 377$$

$$\approx 2 \text{ mH}$$

α cannot go below 0° . Therefore, to calculate the minimum transformer turns ratio a

$$\left(\text{where } a = \frac{V_{pri}}{V_{sec}} \right), \text{ in Eq. 6-26}$$

$$V_d = \frac{0.9}{a} V_s \cos \alpha - \frac{2}{\pi} \omega (L_s) I_d$$

In a rigorous calculation, this should be $\left(\frac{L_s}{a^2} \right)$

$$\text{Substitute } V_d = 100 \text{ V}, \quad \alpha = 0^\circ \text{ and } V_s^{\min} = 115 \text{ V} (-10\%) = 103.5 \text{ V}$$

$$\therefore \text{ From the above Eq: } a_{\text{minimum}} \approx 0.89$$

$$\text{With } a_{\text{minimum}} \text{ and } V_s = 115 \text{ V} (+5\%) = 120.75 \text{ V},$$

$$\text{the above Eq yields } \alpha = 31^\circ \text{ for } V_d = 100 \text{ V.}$$