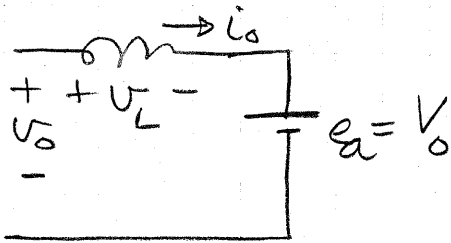


Problem 7-23

In the circuit of Fig 7-27, $R_a \approx 0$. Consider the waveforms in Fig. 7-29 under steady state.



during D_{on} : T_{A+} , T_{B-} ON

$$\Delta I_L = \frac{V_d - V_o}{L_a} D_{on} T_s$$

From the Waveform of V_o :

$$2 V_d D_{on} = V_o$$

$$\therefore D_{on} = \frac{1}{2} \frac{V_o}{V_d}$$

$$\therefore \Delta I_L = \frac{T_s V_d (1 - \frac{V_o}{V_d})}{2 L_a} \frac{V_o}{V_d}$$

$$\frac{\partial(\Delta I_L)}{\partial(\frac{V_o}{V_d})} = \frac{T_s V_d}{2 L_a} \left[-\frac{V_o}{V_d} + (1 - \frac{V_o}{V_d}) \right] = 0 \quad (\text{set to})$$

\therefore maximum occurs at $\frac{V_o}{V_d} = \frac{1}{2}$.

Using $\frac{V_o}{V_d} = \frac{1}{2}$ in the equation for ΔI_L ,

$$\begin{aligned} (\Delta I_L)_{\text{maximum}} &= \frac{T_s V_d}{2 L_a} \left(\frac{1}{2} \right) \left(\frac{1}{2} \right) = \frac{T_s V_d}{8 L_a} \\ &= \frac{V_d}{8 L_a f_s} \end{aligned}$$